

ENED 1200 – Spring 2024

Homework 11.1: VBA 2 (Conditional)

INDIVIDUAL ASSIGNMENT: See the course syllabus for a definition of what constitutes an individual HW assignment.

Task 1 (of 1): Resistors, Voltages, and Currents

Kirchhoff's Laws

Kirchhoff's laws are fundamental principles in electrical circuit theory named after Gustav Kirchhoff, a German physicist. These laws are crucial for analyzing and solving electrical circuits. These laws have implications for circuits with resistors connected in series or parallel.

Series Resistors:

Kirchhoff's Current Law (KCL) states that **the total current entering a junction in a circuit must equal the total current leaving the junction**, which implies that the current is constant in a series circuit. Therefore, according to KCL, the current across each resistor in a series circuit will remain constant.

The equivalent or **total resistance of a series combination** can be found with the following equation.

$$R_{\text{total}} = \sum R_i = R_1 + R_2 + \dots$$

The Voltage on an individual resistor, if the source Current is known, can be found with the following equation.



$$V_{R_i} = I_s \cdot R_i \quad (\text{We can use } R_{\text{Total}} \text{ and } V_s \text{ to find } I_s)$$

Parallel Resistors:

In a parallel circuit, the voltage across each branch remains constant. This is in accordance with Kirchhoff's Voltage Law (KVL), which states that the sum of the voltages around any closed loop in a circuit is equal to zero. Since each branch in a parallel circuit forms a closed loop, the voltage across each branch remains constant regardless of the current flowing through it.

The equivalent or **total resistance of a parallel combination** can be found with the following equation.
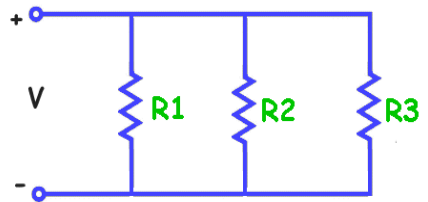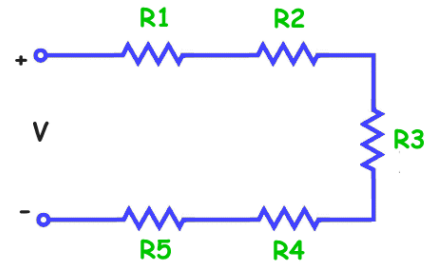
$$R_{\text{total}} = \frac{1}{\sum \frac{1}{R_i}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots}$$



If there are only two resistors in parallel, a shortcut equation can be used to find the equivalent resistance.

$$R_{\text{total}} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

Current on an individual resistor if source Voltage is known can be found with the following equation.

$$I_{R_i} = \frac{V_s}{R_i}$$

Your VBA Conditional Task

Please use the provided starter file, **HW_11p1_VBA2_Task1.xlsm** on the community page to develop a **Macro called Kirchhoff** that asks users to input either **2 or 5 Resistor values**, and the source Voltage to find out the Resultant Resistance, and Voltage and Current through each individual Resistor.

Please follow these steps:

- Declare your variables.
- Clear the output cells from previous data. use `ActiveSheet.Cells(4, 11) = ""` to clear individual cell and `ActiveSheet.Range("Provide the range of cells").ClearContents` to clear a range of cells.
- Ask the user for the inputs. For the resistors, they must either enter 2 resistors or 5. If they enter any other value, it may cause a division by zero error. For example, if they enter 4 values, the program will be expecting 5 values and will automatically assign the 5th Resistor a “zero”.
- **Make a count** of how many resistor values are entered. **Please use this worksheet function: `Count = WorksheetFunction.Count(Range("D4:D8"))`**
- Ask users to select either “Series” or “Parallel” circuits with the data validator in the G10 cell.
- While calculating the outputs, there are total five conditions to check. 1 and 2: If the count is 2 or 5 and the circuit is in Parallel. 3 and 4: if the count is 2 or 5 and the circuit is in Series. 5: if there is a different number of Resistors, **display a MsgBox saying “ Please enter values for either 2 or 5 Resistors”**.
- Use the appropriate equations while remembering that Current remains constant through Series circuits while Voltage remains constant through Parallel circuits.

Test Cases

Inputs: Voltage = 5V, R1 = 2Ω, R2 = 3Ω, R3 = 4Ω, R4 = 5Ω, R5 = 6Ω

Outputs: Series: R_Total = 20Ω, R1 = 0.5Ω, R2 = 0.75Ω, R3 = 1Ω, R4 = 1.25Ω, R5 = 1.5Ω.

Current same for all = 0.25A

Parallel: R_Total = 0.69Ω, R1 = 2.50Ω, R2 = 1.67Ω, R3 = 1.25Ω, R4 = 1Ω, R5 = 0.83Ω.

Voltage same for all: 5V

Submit the file to your section site with the following name:

HW_11p1_VBA2_Task1_UCusername.xlsm where *UCusername* is your 6+2.